

EXPERIMENT - 1

VERIFICATION OF KCL AND KVL


Aim: To verify KCL and KVL for given DC circuit

Apparatus: (1) 0-30V, 2A regulated dc power supply - 1 No,
(2) 0-30V voltmeters - 3 Nos, 0-2A Ammeters - 3 Nos

50 Ω /2A, 100 Ω /2A, 150 Ω /2A Rheostat 1 No each

Verification of KVL

Circuit diagram:-

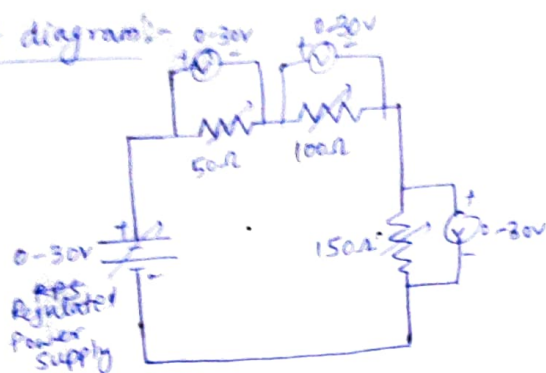

Tabular Column:-

S.No	R.P.S Vtg	V_1 (V)	V_2 (V)	V_3 (V)	$V = V_1 + V_2 + V_3$
1.	10V	2V	3V	4.5V	$10 = 2 + 3 + 4.5$
2.	15V	3V	5V	7V	$15 = 3 + 5 + 7$
3.	20V	4V	6V	10V	$20 = 4 + 6 + 10$
4.	25V	5V	8V	12V	$25 = 5 + 8 + 12$
5.	30V	5V	10V	14.5V	$30 = 5 + 10 + 14.5$


Result:-

For the given DC circuit, KVL is verified.

Signature

Verification of KCL

Circuit Diagram:-

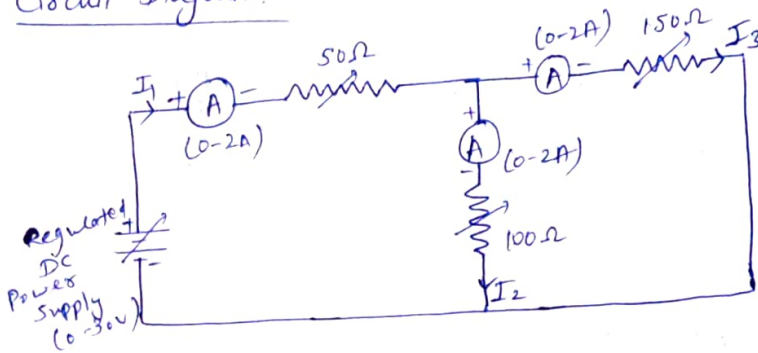

Tabular Column:-

Sl. No.	R.P.S Vtg	$I_1(A)$	$I_2(A)$	$I_3(A)$	$I_1 = I_2 + I_3$
1.	10V	0.35A	0.25A	0.10A	$0.35 = 0.25 + 0.10$
2.	15V	0.6A	0.4A	0.2A	$0.6 = 0.4 + 0.2$
3.	20V	0.75A	0.50A	0.25A	$0.75 = 0.5 + 0.25$
4.	25V	0.9A	0.65A	0.35A	$1 = 0.65 + 0.35$
5.	30V	1.2A	0.8A	0.4A	$1.2 = 0.8 + 0.4$

Result:-

For the given DC circuit, KCL is verified.

Signature
13/1/22

20/01/22


EXPERIMENT-2

POWER

MEASUREMENT OF CURRENT, PF OF INCANDESCENT LAMP, FLUORECENT LAMP

Aim:- To measure current, power and power factor of incandescent lamp, fluorescent lamp and LED lamp.

Circuit Diagram:-

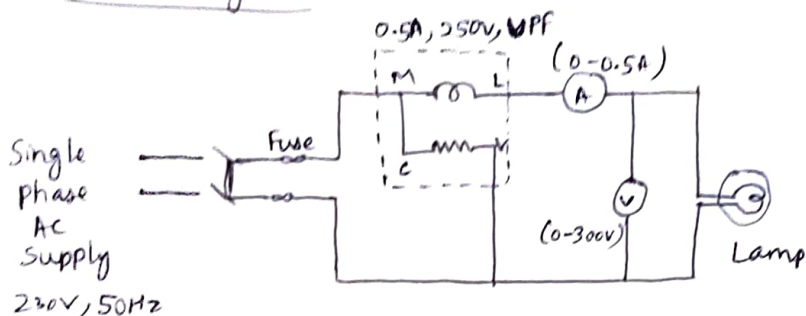

Tabular Column:-

S.No	Lamp	V	I	P	P.F	
					Measured	Calculated
1.	Incandescent	224.5V	0.169A	37.7W	0.996	0.993
2.	CFL	225V	0.038A	7.250W	0.940	0.847
3.	LED	225.2V	0.035A	6.897W	0.952	0.875

Calculations:-

$$P = VI \cos \phi$$

$$P.F = \cos \phi = \frac{P}{VI}$$

$$\text{For Incandescent lamp} = \frac{37.7}{224.5 \times 0.169} = 0.993W$$

$$\text{For fluorescent lamp} = \frac{7.250}{225 \times 0.038} = 0.847W$$

$$\text{For LED lamp} = \frac{6.897}{225.2 \times 0.035} = 0.875W$$

Result:-

Measured current, power and power factor of incandescent, fluorescent and LED lamp successfully.

Incandescent is ~~observing~~ ^{consuming} more power.

LED is consuming less power.

20/01/22


EXPERIMENT - 3

20/01/22

Maximum power Transfer Theorem

Aim:- To determine maximum power transferred from source to the load when the internal resistance is equal to load resistance.

Circuit Diagram:-

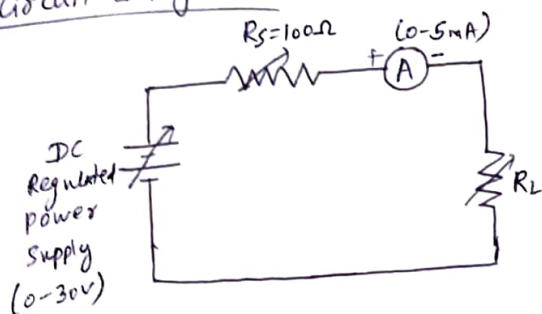

Tabular Column

$V = 25V$ $R_S = 105\Omega$

Sl. No	R_L in Ω	I_A in mA	$P = I^2 R_L$ in W
1.	10	0.32 A	1.024 W
2.	20	0.29 A	1.682 W
3.	30	0.26 A	2.028 W
4.	40	0.24 A	2.304 W
5.	50	0.22 A	2.420 W
6.	60	0.21 A	2.646 W
7.	70	0.19 A	2.527 W
8.	80	0.18 A	2.592 W
9.	90	0.17 A	2.601 W
10.	100	0.16 A	2.560 W
11.	110	0.16 A	2.816 W
12.	120	0.15 A	2.700 W
13.	130	0.14 A	2.548 W
14.	140	0.13 A	2.366 W
15.	150	0.13 A	2.535 W
16.	160	0.12 A	2.304 W

Result:- By Maximum power transfer theorem, source resistance is equal to load resistance.

$$R_S = R_L = 110\Omega$$


$$P_{max} = 2.8W$$

20/01/22

Condition for Maximum power transfer:

$$R_S = R_L$$

Model Graph:

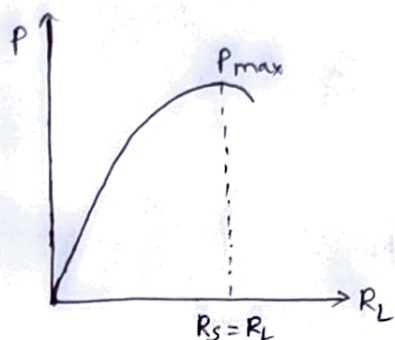


7/01/22

EXPERIMENT - 4

TWO WAY AND THREE WAY CONTROL OF LAMP

Aim:- To conduct two way and three way control of lamp using switches in single phases circuit.

Two way Control of Lamp

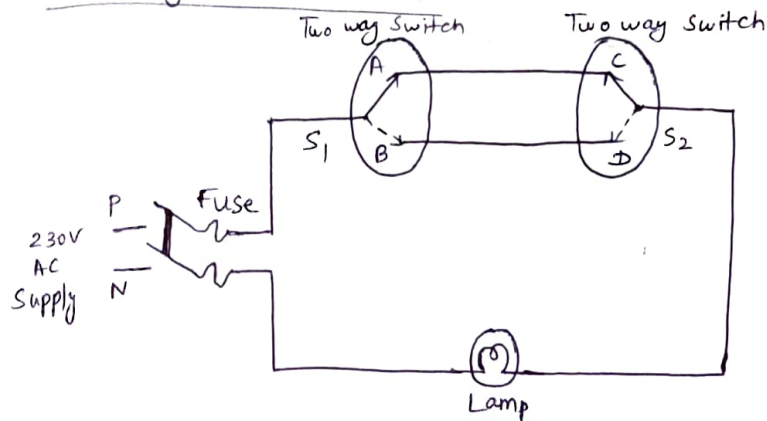


Tabular Column:-

Sl. No	Switch S ₁	Switch S ₂	Condition of Lamp Analysis	Condition of Lamp Observer	Tracing the Path
1.	A	C	ON	ON	P-A-C-Lamp-N
2.	A	D	OFF	OFF	—
3.	B	D	ON	ON	P-B-D-Lamp-N
4.	B	C	OFF	OFF	—

Three way Control

Circuit Diagram:-

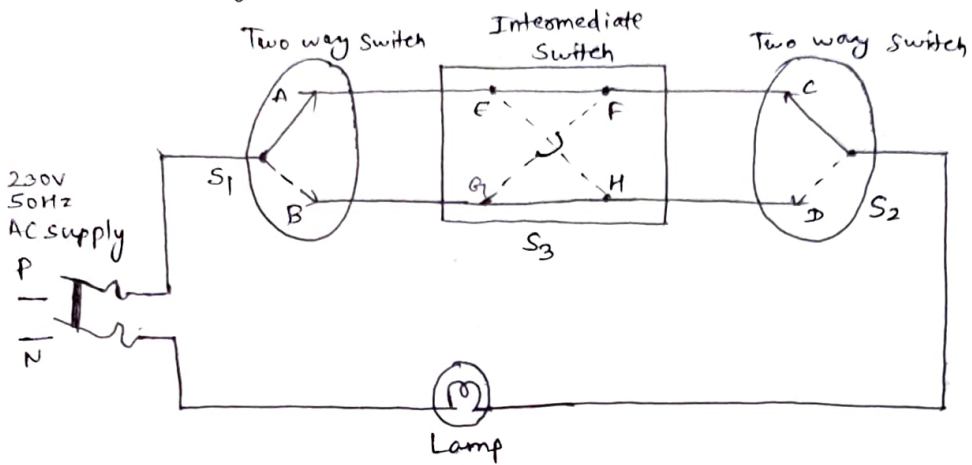

Tabular Column:-

Sl. No.	Switch S_1	Switch S_2	Switch S_3	Condition of Lamp Analysis	Condition of Lamp Observer	Tracing the Path
1.	A	C	EF, GH	ON	ON	P-A-EF-C-Lamp-N
2.	A	D	EF, GH	OFF	OFF	-
3.	B	D	EF, GH	ON	ON	P-B-GH-D-Lamp-N
4.	B	C	EF, GH	OFF	OFF	-
5.	B	C	EH, GF	ON	ON	P-B-GF-C-Lamp-N
6.	B	D	EH, GF	OFF	OFF	-
7.	A	D	EH, GF	ON	ON	P-A-EH-D-Lamp-N
8.	A	C	EH, GF	OFF	OFF	-

Result:-

Conducted experiment on two way and three way control of lamp using switches in single phase circuit and verified the truth table successfully.


[Signature]
17/2/22

EXPERIMENT - 5

Measurement of Resistance and Inductance of a Choke by Three Voltmeter Method

Aim:- To measure the resistance and inductance of a choke coil using three voltmeter methods.

Circuit Diagram:-

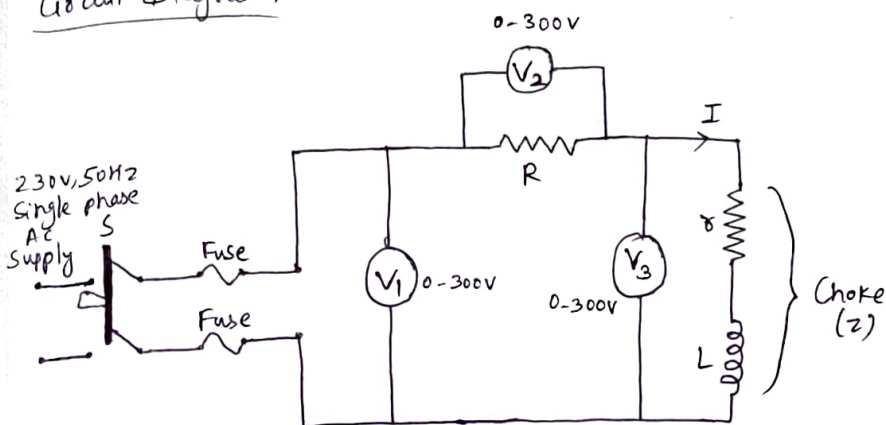

Tabular Column:-

$$R = 472 \Omega$$

Sl No.	V_{supply} (Volts) V_1	V_{choke} (Volts) V_3	V_R (Volts) V_2	Current (I) (Amps)	$\cos \phi$	L (Henry)	δ (Ω)
1.	100.6V	25.94V	93.32V	0.197A	0.152	0.414H	20.014 Ω
2.	150.7V 150.4V	39.62V	139.7V	0.296A	0.146	0.421H	19.544 Ω
3.	200.4V	52.91V	186.3V	0.394A	0.134	0.423H	17.995 Ω

Calculations:-

$$1) V_{\text{supply}} = V_1 ; V_R = V_2 ; V_{\text{choke}} = V_3$$

$$V_{\text{supply}} = \sqrt{V_R^2 + V_{\text{choke}}^2 + 2 V_R V_{\text{choke}} \cos \phi}$$


$$\cos \phi = \frac{V_{\text{supply}}^2 - V_R^2 - V_{\text{choke}}^2}{2 V_R V_{\text{choke}}}$$

$$2) I = \frac{V_R}{R} =$$

$$R = 472 \Omega$$

$$3) Z_{\text{choke}} = \frac{V_{\text{choke}}}{I}$$

4)

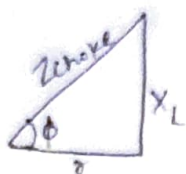

$$r = Z_{\text{choke}} \cos \phi$$

$$X_L = Z_{\text{choke}} \sin \phi$$

$$X_L = 2\pi fL$$

$$L = \frac{X_L}{2\pi f}$$

5) L_1, L_2, L_3

r_1, r_2, r_3

$$L = \frac{L_1 + L_2 + L_3}{3}$$

$$r = \frac{r_1 + r_2 + r_3}{3}$$

Result:- Measured the resistance and inductance of a choke coil using three voltmeter method successfully.

Resistance (R) = 19.184Ω

Inductance (L) = 0.419 H


Signature
17/2/22

7/02/22

EXPERIMENT-6Measurement of Earth Resistance

Aim:- To measure earth resistance of an installation with the help of ^{Earth} tester.

Circuit Diagram:-

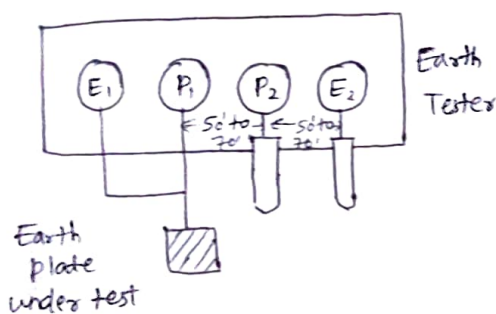

Tabular Column:-

S No	Earth Resistance (Ω)
1.	2.33
2.	4.03
3.	2.07
4.	1.36
5.	2.13
6.	4.33

$$\text{Earth resistance} = 2.708 \Omega$$

Result:- Measured earth resistance of an installation with the help of ^{Earth} tester.

$$\text{Earth resistance} = 2.708 \Omega$$

Signature
17/2/22


03/03/22

EXPERIMENT-7

Determination of phase and line quantities in 3 ϕ star and delta loads

Aim:- To determine the relationship b/w the phase quantities and line quantities in star and delta connected three phase system.

Circuit diagram:- (Star connected)

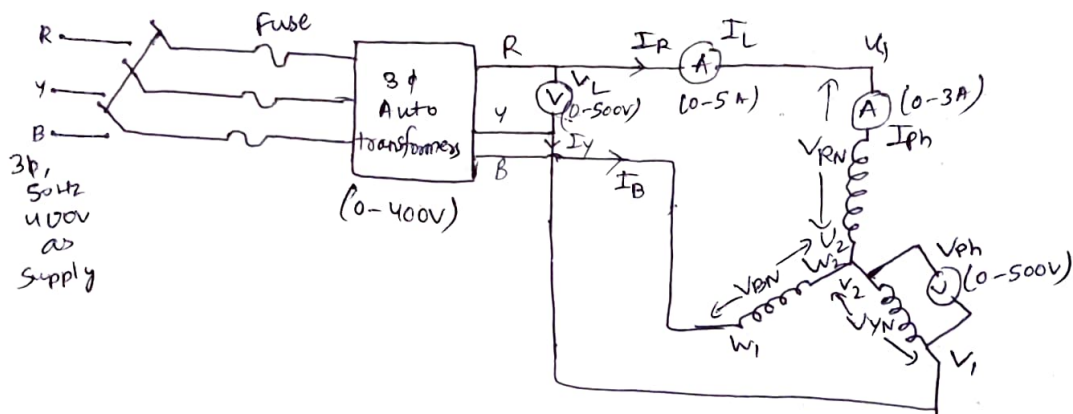

Tabular Column:-

Sl	I_L (A)	I_{ph} (A)	V_{ph} (V)	V_L	
				Measured	Calculated
1.	0.332	0.333	231.1	401.6	400.2
2.	0.665	0.667	231.3	401.7	400.6
3.	1.001	1.002	231.2	401.4	400.45

Calculation:-

$$\frac{I_L}{I_{ph}} = 1 \Rightarrow \frac{0.332}{0.333} \approx 1$$


$$V_L = \sqrt{3} V_{ph}$$

$$400.2 = \sqrt{3} \times 231.1$$

$$400.6 = \sqrt{3} \times 231.3$$

$$400.45 = \sqrt{3} \times 231.2$$

Delta Connected load

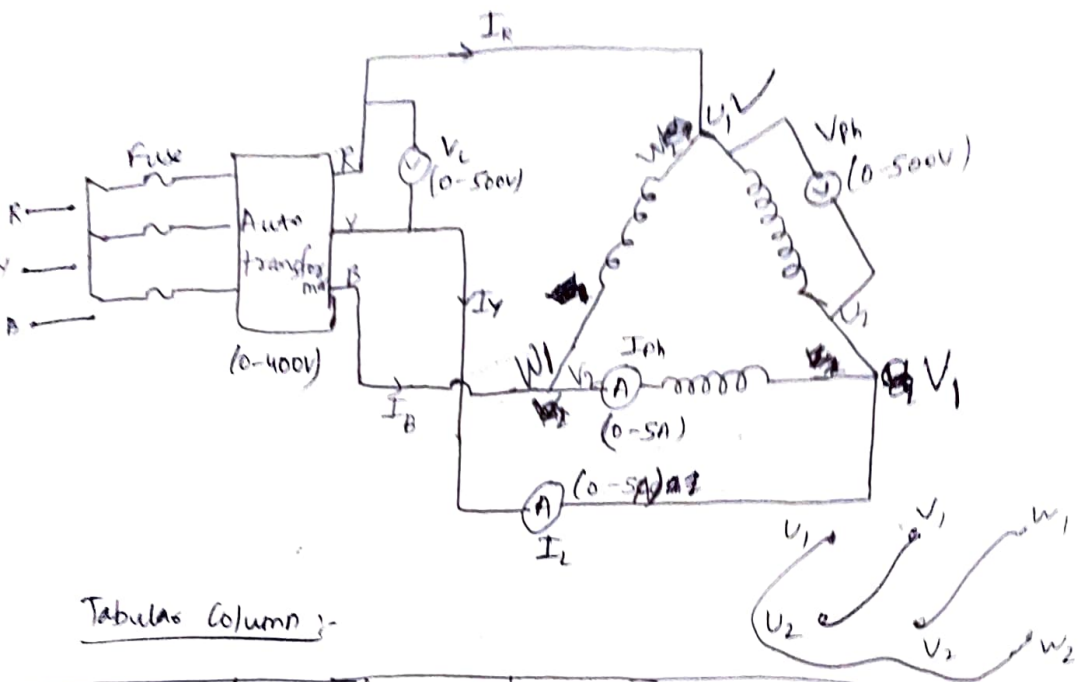

Tabular Column :-

Sl.	V_L (V)	V_{ph} (V)	I_{ph} (A)	I_L (A)	
				Measured	Calculated
1.	402.4	401.4	0.582	1.008	1.008
2.	402.3	401.1	1.164	2.013	2.016

Result:- Determined the relationship b/w the phase and line parameters in star & delta connected load.

For star connected, $V_L = \sqrt{3} V_{ph}$, $I_L = I_{ph}$

For delta connected, $I_L = \sqrt{3} I_{ph}$, $V_L = V_{ph}$

Calculation:-

$$\frac{V_L}{V_{ph}} = 1 \quad \frac{402.4}{401.4} \approx 1$$

$$I_L = \sqrt{3} I_{ph}$$

$$1.008 = \sqrt{3} \times 0.582$$

$$2.016 = \sqrt{3} \times 1.164$$

3/3/22